

Summary: All Four Topology Matrices

Building Blocks for State-Space Averaged Model

Topology 11 (Both ON - Storage)

A11: Rows 1-6: Direct charging (L1, L2), reverse (L5, L6)
Row 7: $dvC1/dt = (-iL5)/C1$
Row 8: $dvC3/dt = (-iL6)/C3$
Row 9: $dvC0/dt = 0$ (CPL separate)

Key: L1, L2 charge from Vin (no cap voltage)
L5, L6 reverse charge through C1, C3
Output isolated (no power transfer)

Topology 10 (S1 ON, S2 OFF)

A10: Row 1: L1 discharges via $-vC3$, $-vC0$
Row 2: L2 direct charging
Row 5: L5 reverse via $-vC1$
Row 6: L6 forward via $+vC0$
Row 7: $dvC1/dt = (-iL5)/C1$
Row 8: $dvC3/dt = iL1/C3$
Row 9: $dvC0/dt = (iL1+iL6)/C0$

Key: Phase 1 stores, Phase 2 transfers
L1, L6 both contribute to output

Topology 01 (S1 OFF, S2 ON)

A01: Row 1: L1 direct charging
Row 2: L2 discharges via $-vC1$, $-vC0$
Row 5: L5 forward via $+vC0$
Row 6: L6 reverse via $-vC3$
Row 7: $dvC1/dt = iL2/C1$
Row 8: $dvC3/dt = (-iL6)/C3$
Row 9: $dvC0/dt = (iL2+iL5)/C0$

Key: Phase 2 stores, Phase 1 transfers
L2, L5 both contribute to output
Symmetric to Topology 10

Topology 00 (Both OFF - Max Transfer)

A00: Rows 1-2: Both L1, L2 discharge
Rows 5-6: Both L5, L6 forward via $+vC0$
Row 7: $dvC1/dt = iL2/C1$
Row 8: $dvC3/dt = iL1/C3$
Row 9: $dvC0/dt = (iL1+iL2+iL5+iL6)/C0$

Key: Both phases transfer simultaneously
ALL FOUR active inductors contribute
Maximum power delivery mode

Key Pattern Observations

- **Capacitor charging:** C1 charges from $iL2$ (when S1 OFF) or $-iL5$ (when S1 ON). C3 charges from $iL1$ (when S2 OFF) or $-iL6$ (when S2 ON).
- **Output current sources:** Topology 11: none (isolated). Topology 10/01: 2 inductors. Topology 00: 4 inductors.
- **Reverse vs. Forward:** When switch ON, output inductor reverse charges (negative current). When switch OFF, it discharges forward (positive contribution to output).
- **These 4 matrices are averaged:** $A_{avg} = W_{11} \cdot A_{11} + W_{10} \cdot A_{10} + W_{01} \cdot A_{01} + W_{00} \cdot A_{00}$ (next slide explains w_k weights)