

# Level 3: Small-Signal Linearization

## From Nonlinear Averaged Model to Linear Transfer Functions

### Why Linearize? Unlocking Linear Control Theory

**Challenge:** The averaged model is still nonlinear due to:

- CPL load:  $f_{CPL} = -P/(C_0 \cdot v_{C0})$  (nonlinear in  $v_{C0}$ )
- Duty cycle dependencies in  $A_{avg}(d1, d2)$

**Solution:** Linearize around a DC operating point to use powerful linear control design tools:

- Bode plots for frequency response analysis
- Root locus for pole placement
- Standard PI/PID controller tuning methods

### Step 1: Perturbation About Operating Point

Nonlinear averaged model:  $\dot{x} = f(x, d1, d2, V_{in})$

Decompose each variable:  $x = x_0 + \Delta x, \quad d1 = d_{10} + \Delta d1, \quad \text{etc.}$

At steady state:  $0 = f(x_0, d_{10}, d_{20}, V_{in0})$

Operating point  $(x_0, d_{10}, d_{20}, V_{in0})$  found via fsolve (MATLAB) or Newton-Raphson

### Step 2: Jacobian Linearization

Taylor series expansion:  $f(x_0+\Delta x, d_{10}+\Delta d1, \dots) \approx f(x_0, d_{10}, \dots) + \frac{\partial f}{\partial x} \Delta x + \frac{\partial f}{\partial d1} \Delta d1 + \dots$

**State Jacobian ( $A_{linear}$ ):**

$A_{linear} = \frac{\partial f}{\partial x} \big|_{(x_0, d_{10}, d_{20}, V_{in0})} = A_{avg}(d_{10}, d_{20}) + \frac{\partial f_{CPL}}{\partial x}$

**CPL Term Derivative (critical for stability):**

$f_{CPL}(v_{C0}) = -P/(C_0 \cdot v_{C0}) \rightarrow \text{row 9 of } f$

$\frac{\partial f_{CPL}}{\partial v_{C0}} = \frac{\partial}{\partial v_{C0}} [-P/(C_0 \cdot v_{C0})] = -P/(C_0) \cdot (-1/v_{C0}^2) = +P/(C_0 \cdot v_{C0}^2)$

Therefore:  $A_{linear}(9,9) = 0 + P/(C_0 \cdot v_{C0_0}^2)$  (POSITIVE term  $\rightarrow$  destabilizing)

### Step 3: Control Input Jacobian ( $B_d$ )

$B_d$  represents how duty cycle perturbations affect state derivatives

$B_d = [\frac{\partial f}{\partial d1} \mid \frac{\partial f}{\partial d2}] \big|_{(x_0, d_{10}, d_{20}, V_{in0})} \quad (9 \times 2 \text{ matrix})$

**Chain rule (duty cycles affect  $A_{avg}$  and  $B_{in,avg}$ ):**

$\frac{\partial f}{\partial d1} = (\frac{\partial A_{avg}}{\partial d1}) \cdot x_0 + (\frac{\partial B_{in,avg}}{\partial d1}) \cdot V_{in0}$

$\frac{\partial f}{\partial d2} = (\frac{\partial A_{avg}}{\partial d2}) \cdot x_0 + (\frac{\partial B_{in,avg}}{\partial d2}) \cdot V_{in0}$

(Derivatives of  $w_k$  w.r.t.  $d1, d2$  propagate through weighted sum)

### Step 4: Linearized Model and Transfer Functions

**Small-signal model:**

$\Delta \dot{x} = A_{linear} \cdot \Delta x + B_d \cdot [\Delta d1; \Delta d2] + B_{in} \cdot \Delta V_{in}$

**Transfer functions (Laplace domain):**

$G(s) = C \cdot (sI - A_{linear})^{-1} \cdot B_d$

Example:  $G_{vd1}(s)$  = output voltage to duty  $d1 \rightarrow C = [0 \ 0 \ 0 \ 0 \ 0 \ 0 \ 0 \ 0 \ 1]$

### Control Design Applications

- $G_{id}(s)$ : duty  $\rightarrow$  input current (inner loop for PFC, tracks AC reference)
- $G_{vd}(s)$ : duty  $\rightarrow$  bus voltage (outer loop for regulation)
- PI/PID tuning via Bode plots, phase/gain margins
- Stability assessment: check poles of  $(sI - A_{linear})^{-1}$  for LHP (stable)

**Critical Insight:** The CPL term  $+P/(C_0 \cdot v_{C0_0}^2)$  in  $A_{linear}(9,9)$  acts as negative incremental resistance, potentially pushing poles toward RHP (instability). Control design must provide sufficient damping to counteract this destabilizing effect, especially at high power loads.